

## ► A Low-Noise Measurement Preamp

By Dennis Colin

Gain of 1000 or 10,000, calibrated noise bandwidths including “A” weighting, and a low noise figure with low and high source resistances facilitate accurate measurements of noise and sub-microvolt signals.

The preamp as shown in **Photos 1-5** is in a Hammond 1590C box (4.72” × 3.70” × 2.07”), which is tightly packed inside (not shown) with the circuitry on a solid copper ground plane board. I recommend the larger Hammond 1590D (7.38” × 4.70” × 2.05”), Digi-key HM154.

The circuit (**Fig. 1A**) uses a low-noise dual (paralleled) JFET (Q1), the Linear

Systems LSK389B (see ads in *aX*) in a feedback configuration with the low-noise AD797AN op amp (U1) for the input stage. This provides very low input voltage noise (about 1nV/√Hz density, 148nV 20Hz – 20kHz noise, 112nV “A” weighted), negligible current noise, and very stable gain (100 = 40dB).



PHOTO 1: Low-noise preamp.

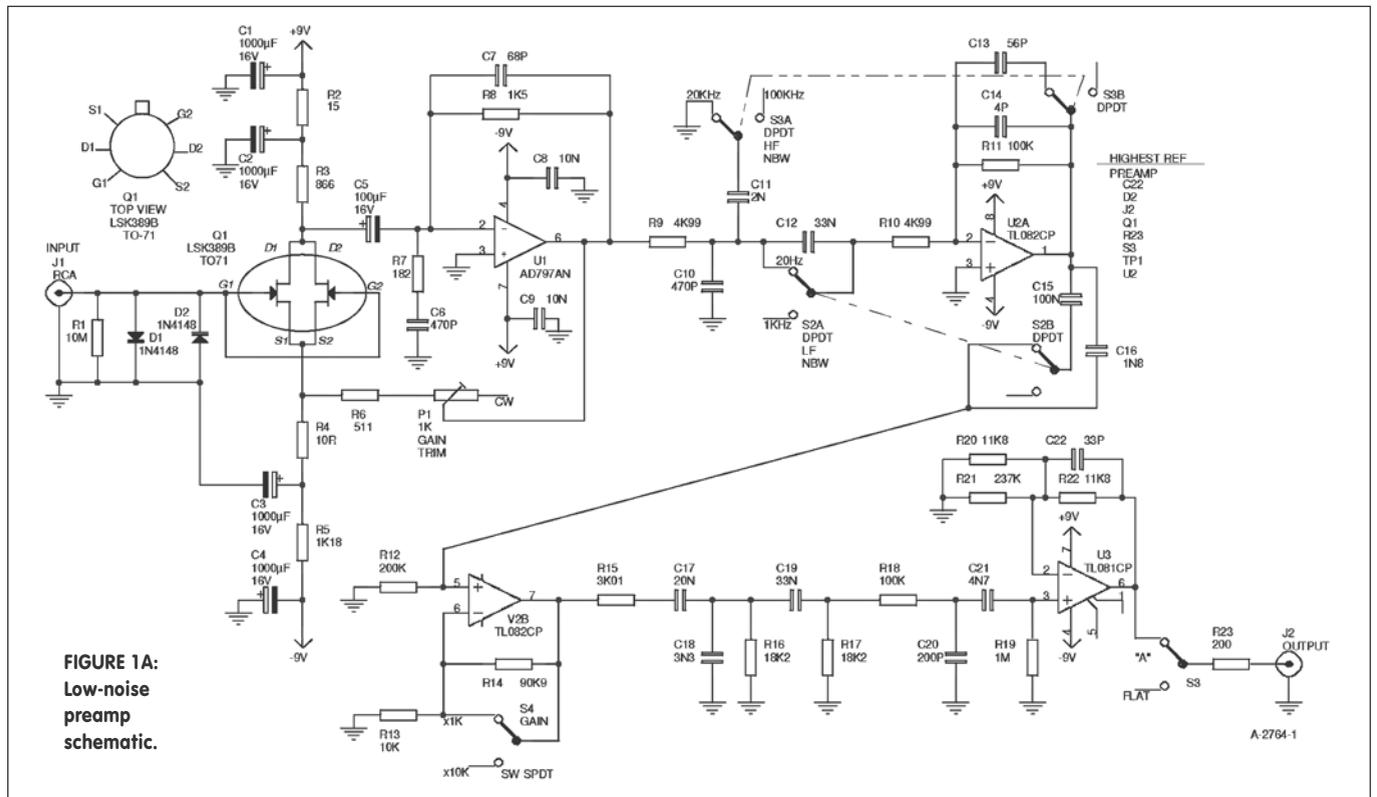


FIGURE 1A:  
Low-noise  
preamp  
schematic.

## EQUIVALENT NOISE BANDWIDTH

**Table 1** shows the noise bandwidth (NBW) of several common low and high-pass filters. NBW means the LF or HF cut-off of an ideal “brick wall” filter that would, with white noise input (constant power per Hz BW), output the same total noise RMS voltage as the actual filter being considered.

The preamp has the following NBW selections:

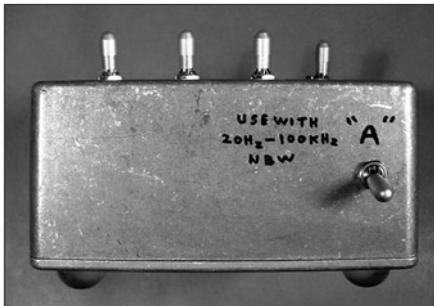


PHOTO 2: Front.

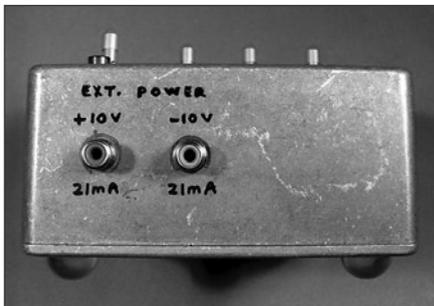


PHOTO 3: Rear.

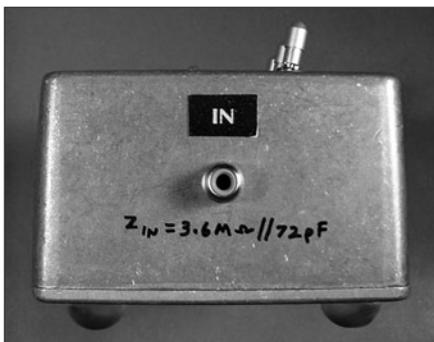


PHOTO 4: Left side.



PHOTO 5: Right side.

1. LF points of 20Hz or 1kHz.
2. HF points of 20kHz or 100kHz.
3. “A” weighting: when used with the above NBW switches in the 20Hz – 100kHz positions, the response is within +0.5, –0.8B of the standard curve shown in **Fig. 6**.

The gain at 1kHz is within  $\pm 0.1$ dB of that with the “A” weighting switch off.

“A” weighting is used in signal/noise ratio (SNR) measurements because it’s a good approximation to our low-level hearing response. The 1kHz LFNBW selection, like “A” weighting, greatly attenuates 60/120Hz AC line hum, but unlike the “A” curve, the pass band response is flat. Since 1kHz is only 5% of the audio band, the measurement (with fairly flat noise spectra) is close to 20Hz – 20kHz total noise voltage, and is useful when there’s significant hum contamination. The 100kHz HFNBW selection is provided when a flat audio response is needed, such as for spectrum analysis.

## GAIN

With gain set to 1000 (60dB), microvolts in become millivolts out. With the preamps maximum output of  $\pm 7.2$ V peak, this allows a maximum sine wave of 5.1V RMS. But with typical (Gaussian) noise, 2.4V RMS is the maximum without significant error-producing peak clipping. So with

gain of 1000, the maximum noise input is 2.4mV RMS.

The gain setting of 10,000 (80dB) allows for the most sensitive noise measurements. The preamp’s own “A” weighted input noise of 112nV RMS then outputs 1.12mV, which can be accurately measured on a true-RMS meter such as the Fluke 189 (\$500) or the much less expensive older Fluke 8010A. Noise levels lower than the preamp’s own noise can be calculated by RMS subtracting it out.

## GAIN STABILITY AND NBW VERIFICATION

I connected a precise 1000:1 attenuator to the input, consisting of a series 99.90k and shunt 100.00 $\Omega$  resistive divider, then set the gain with this attenuator to unity. The preamp’s switches were set to gain = 1000, LFNBW = 20Hz, HFNBW = 100kHz, “A” weighting off. The preamp’s gain at 1kHz was then set to 1000  $\pm 0.01\%$  ( $\pm 0.0009$ dB).


Gain change versus supply voltage was +0.037dB per volt. Temperature drift was –0.035dB/ $^{\circ}$ C. Warmup change from 10 seconds to 10 minutes was –0.007dB. Note: After power-on, it takes six seconds for the bias caps to sufficiently charge.


The frequency response plots in **Fig. 2** show the effects of the LF and HF noise bandwidth switches.

**TABLE 1: Noise bandwidth of several non-resonant filters (multiple poles at the same frequency). NBW = equivalent noise cutoff frequency, low or high cut.**

Filter Type	NBW/ pole frequency	dB at pole frequency	dB at equivalent noise cutoff	–3dB frequency/ noise cutoff
1st order LPF	$\pi/2 = 1.5708$	–3	–5.400	$2/\pi = 0.6366$
2nd order LPF (non-resonant)	$\pi/4 = 0.7854$	–6	–4.173	0.8178
3rd order LPF (non-resonant)	$3/16\pi = 0.5890$	–9	–3.881	0.8638
1st order HPF	$\pi/2 = 1.5708$	–3	–1.478	$2/\pi = 0.6366$
2nd order HPF (non-resonant)	$3/4\pi = 2.3562$	–6	–0.719	0.6608

**FIGURE 1B: Power supply schematic.**

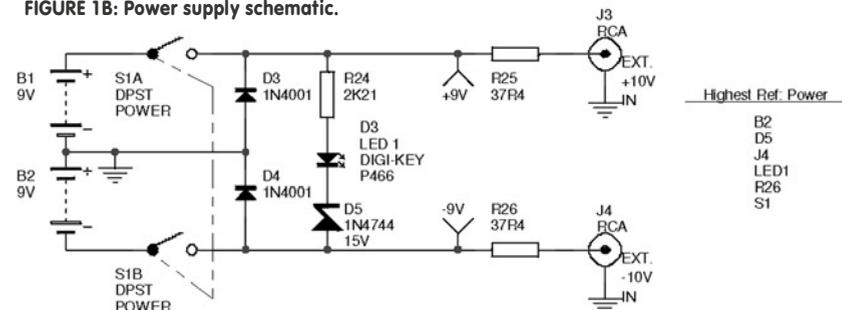

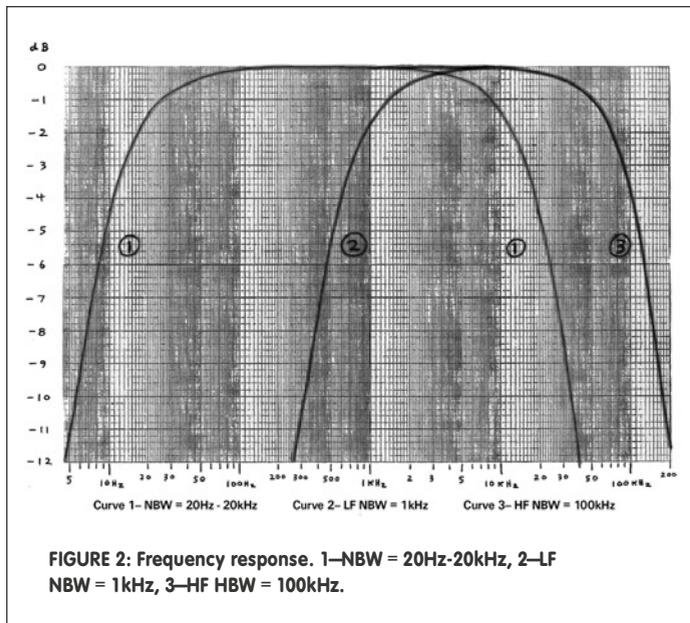

## CIRCUIT

The input is DC-coupled to the JFET gates for lowest noise. D1, D2 protect the JFETs from static discharge, and so on. If an AC-coupled input is desired, I recommend a 100nF 630V film capacitor. I use one installed in a shielded cable assembly, for noise measurements on circuits (such as power supplies) having more than  $\pm 100\text{mV}$  DC (the maximum allowable without a blocking cap). The series 100nF cap increases the preamp's 20Hz – 1kHz noise floor by about 0.4dB.

Input impedance is  $3.6\text{M}\Omega/33\text{pF}$ . This capacitance is low for a JFET input because the drain signal sees the “virtual ground” of U1's inverting input, thus eliminating Miller effect. R7, C6, and C7 ensure HF stability of U1 and the JFET/op amp feedback loop (U1 has a GBW product of 110MHz). R8 provides DC stability of U1.

For lowest noise and spurious pickup, R1, D1, D2, and C3 should have their ground terminals connected to a chassis ground lug on the input jack J1. The output of U1 has a gain of 100 (40dB) re the input, and a –3dB BW of about 10Hz to 500kHz.

## SECOND STAGE

U2A has a gain of 10 (20dB). Switches S2 and S3 select the LF and HF rolloffs corresponding to the selected LF NBW and HF NBW. C15 and C16 also remove accumulated DC offsets.

## THIRD STAGE

U2B has a flat response and selectable gain (by S4) of 1 or 10, for an overall preamp gain of 1000 or 10,000.

different value for R21 (and possibly R20) if you want fractional dB accuracy.

## POWER SUPPLY

Figure 1B shows the simple dual 9V alkaline battery supply used. The relatively high current drain of  $\pm 21\text{mA}$  results in a battery life of about 10 hours. Of course, higher capacity NiCd, NiMH, or lithium ion/polymer batteries can be used. The specified blue LED, with R24 and D5, serves as a low-battery indicator, extinguishing when the batteries discharge to 8.5V.

## EXTERNAL SUPPLY

An AC line powered  $\pm 10\text{V}$  supply can be used if it's ground-isolated. Table 2 shows the preamp's input-referred noise with its batteries or an external LM317/LM337 regulated supply having about  $40\mu\text{V}$  RMS integrated 20Hz – 20kHz noise. Note that the maximum preamp noise increase (0.54dB) is in the 20Hz – 1kHz band. With “A” weighting or a 1kHz LFNBW, the line-supplied preamp noise increase was less than 0.01dB.

## “A” WEIGHTING

The circuitry from U2B output to U3 output is based on that used by Charles Hansen in “Noise Meter Amp” (*aX* Jan. '05), but with higher impedances allowing smaller caps, and some tweaking. I selected R21 for a 1kHz gain match ( $\pm 0.02\text{dB}$ ) re the “flat” position of S5. Depending on “A” network component tolerances, you might need a

An external  $\pm 10\text{V}$  supply has another useful feature: while normally used with the battery switch S1 off, if this is on with the external DC supply, the battery voltages will charge, if needed, tending toward the  $\pm 9.2\text{V}$  that is produced without batteries. This is completely safe, despite the “Do Not Charge” warning on 9V alkaline batteries. I've recharged these often over many years, provided that the current and voltage are safely limited, as they are here with regulated  $\pm 10\text{V}$  applied. The equilibrium level of 9.2V is safely less than the 9.6V typical of a new “9V” alkaline battery. I haven't had one battery explode in over 15 years. But I know, “there's always a first time”—if you're concerned, keep S1 off when using external power.

## POWER SUPPLY REJECTION RATIO

I injected 100mV RMS at 60 and 120Hz into the 10V supplies (using a transformer). With the preamp gain at 1000, and 20Hz – 20kHz NBW, the output ripple from the positive supply was 50.4mV (60Hz) and 13.0mV (120Hz). From the negative supply, the output ripple was 7.3mV (60Hz) and 1.0mV (120Hz). The op amps have excellent PSRR, but not the single-ended JFET input!

The worst-case PSRR (positive supply at 60Hz) is thus about 2, or 6dB, re the output with gain of 1000. This agrees with the lowest row in Table 2, where RMS subtracting the 20Hz – 1kHz noise voltages yields 22.6nV RMS input-referred line ripple. Not bad for an AC line powered supply; 22.6nV is 194.5dB below the all-surrounding 120V AC. 194dB is the brightness ratio of two lightbulbs, one at 3" from your eyes, the other one at the distance of the moon!

## WHAT'S WRONG WITH CONVENTIONAL NOISE MEASUREMENTS?

Nothing's wrong with the numbers plotting noise density (e.g.,  $\text{nV}/\sqrt{\text{Hz}}$ ) versus

**TABLE 2: PREAMP INPUT NOISE.**

NBW	INPUT REFERRED NOISE, RMS		$\Delta$ , AC/batt
	Int. Batteries	Ext. AC/DC supply	
“A” weighted	111.5nV	111.5nV	0.00dB
20Hz-20kHz	147.7nV, 1.045nV/ $\sqrt{\text{Hz}}$	149.4nV	0.10dB
1kHz-20kHz	134.0nV, 0.972nV/ $\sqrt{\text{Hz}}$	134.0nV	0.00dB
1kHz-100kHz	276.5nV, 0.879nV/ $\sqrt{\text{Hz}}$	276.5nV	0.00dB
20kHz-100kHz	241.9nV, 0.855nV/ $\sqrt{\text{Hz}}$	241.9nV	0.00dB
20Hz-1kHz	62.1nV, 1.984nV/ $\sqrt{\text{Hz}}$	66.1nV	0.54dB

frequency. The problem is that such plots don't express the *perceived* level and spectrum, because of three factors:

1. Conventional spectrum analysis uses a constant bandwidth;  $nV/\sqrt{\text{Hz}}$  means the RMS noise in a 1Hz BW. On such a graph, white noise is flat. However, you don't hear this way, but rather on a log frequency basis; e.g., per octave,  $\frac{1}{2}$  octave, and so on. On such a spectrum graph, white noise has a constant upward 3dB/octave slope, and *sounds* "hissy".

That's why *pink noise*—with its constant power per octave sounding like a steady ocean wave noise—is used. On a constant BW plot, pink noise (sonically misleadingly) has a constant downward 3dB/octave slope.

So, the reasonably "white" spectrum of

many audio components (similar to this article's preamp), fairly flat on a per-Hz basis above 1kHz, has that "hissy" sound, heard mostly in the higher frequencies where the ear is most sensitive at the (you hope) quiet levels of component noise.





2. A linear dB (log voltage) vertical scale would be in accordance with your hearing.
3. The "A" weighting curve (for low-level sounds) further emphasizes (perceptually) the mid-treble range; the "A" curve peaks at 2.5kHz, like your low-level hearing (**Fig. 6**).

For phono preamp design, the audibility of the amplified cartridge plus preamp input noise is modified by a fourth factor, the RIAA curve. Fortunately, this strongly attenuates the higher frequencies.

## NOISE SPECTRA OF THIS PREAMP, WITH AND WITHOUT THE ABOVE FACTORS

**Figure 3** shows the unweighted input noise density spectrum. Curve 1 is conventionally plotted, using  $nV/\sqrt{\text{Hz}}$ . Curve 2 shows the same data, but with constant per-octave analysis, the way you hear. Above 1kHz the  $nV/\sqrt{\text{Hz}}$  density is flat within 3.1dB p-p (reasonably "white"); the per-octave curve reflects this as an exponential rise.

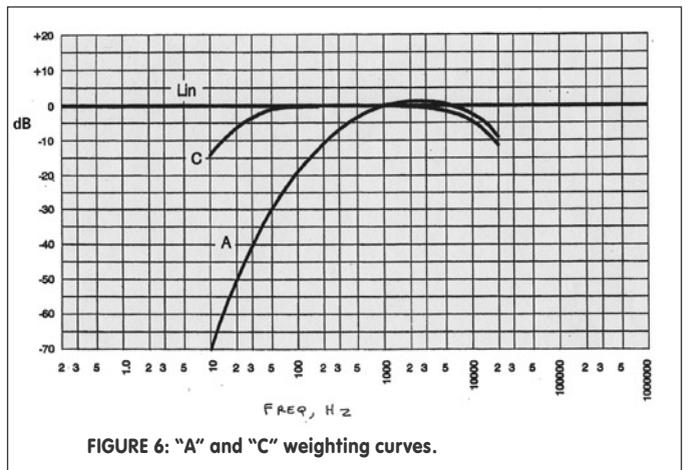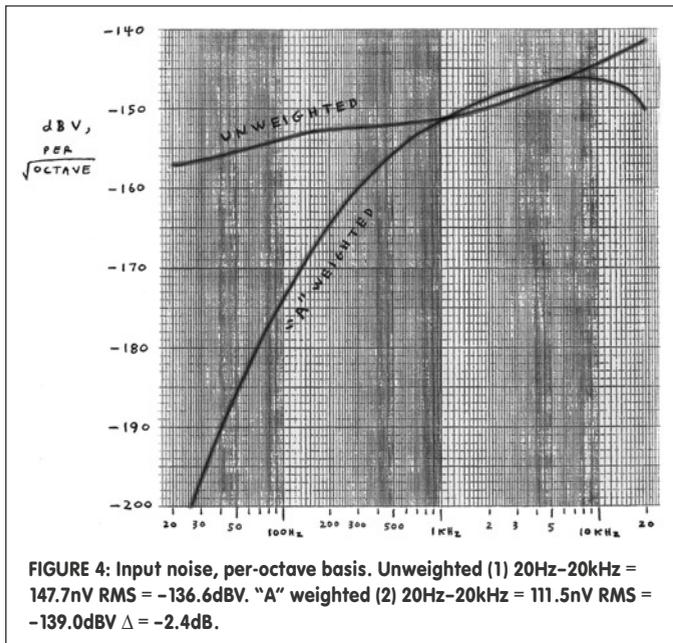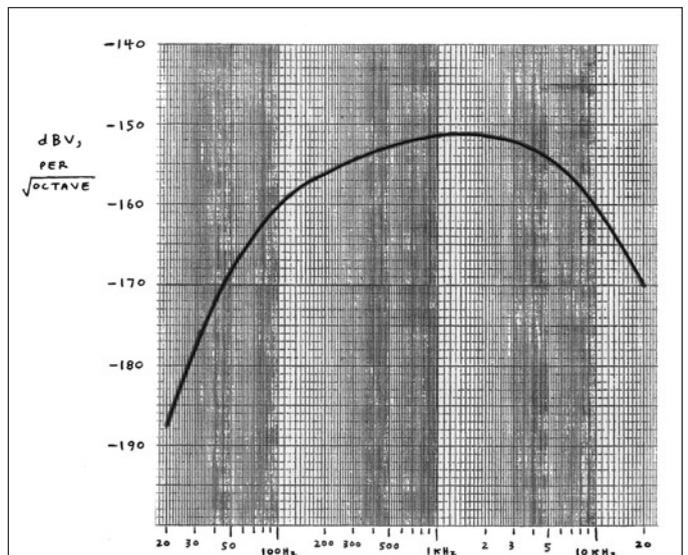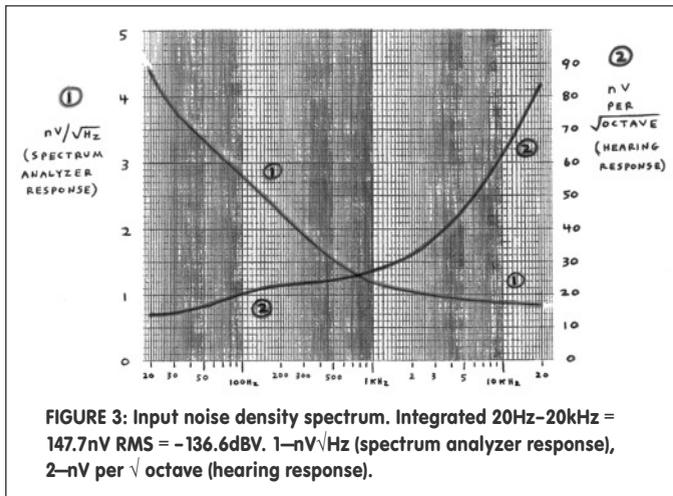The unweighted noise curve in **Fig. 4** shows this as an upward slope approaching 3dB/octave from 1-20kHz. But applying "A" weighting (for low-level sounds) with the dB scale of **Fig. 4** shows the noise spectrum as you hear it. It broadly peaks around 6kHz. Note that "A" weighting reduces the integrated 20Hz – 20kHz noise level by only 2.4dB, whereas some components might



show an 8dB or so reduction.

This has nothing to do with the per-octave analysis; noise power is noise power no matter how it's (accurately) measured. To see why the reduction here is only 2.4dB involves the following:

1. The "raw" ( $nV/\sqrt{Hz}$ ) spectrum in **Fig. 3** curve 1 has a strong LF rise below 1kHz. With the log frequency scale, this appears to affect half the spectrum. But 1kHz is only 5% of the 20kHz audio (and noise) BW. That's why the audio band averaged noise density is only  $1.045nV/\sqrt{Hz}$ , about the level at 2kHz. The "A" curve mostly attenuates below 1kHz (**Fig. 6**), again affecting only 5% of the audio band.
2. Notice in **Fig. 6** that at the peak frequency of 2.5kHz, the "A" curve is 1.1dB higher than the flat ("Lin") reference for loud sounds. Apparently, this reflects the ear's maintaining high sensitivity from 1-5kHz down to the quietest audible SPL. In any case, with noise having strong 1-5kHz content (such as white or near-white noise), you can see that the "A" weighting curve doesn't reduce the overall noise level much.
3. Often, the significant "A" weighting reduction of a component's "noise" is due to that "noise" containing significant 60/120Hz power line hum (and harmonics). When you're considering nanovolts of noise per Hz BW, it doesn't take much discrete-frequency hum to dominate the raw measured noise + hum power. But, of course, the hum, being of low frequency and (you hope) low level compared to the audio signal, is greatly attenuated by the "A" curve (28dB at 60Hz, 17dB at 120Hz) and by your low-level hearing.

## THE RIAA CURVE INFLUENCE

**Figure 5** shows the preamp's input noise spectrum when all four appropriate factors are considered: per-octave hearing, linear dB (logarithmic) hearing, the "A" curve, and the downward-sloping RIAA curve. Note that here the noise has a broad peak around 1.5kHz, with strong LF and HF attenuation. Consequently, the perceived noise reduction is 6.8dB with regard to the raw input

noise.

Therefore, with a typical near-white input noise distribution above 1kHz, the phono preamp's output SNR will be about 6.8dB better than the raw input noise level would indicate. Phono preamp designers, remember that number! (I just built one, the "LP797"; that number is close.)

For non-RIAA components, the SNR improvement is about 2.4dB.

## MEASURING PERCEIVED NOISE LEVEL

1. Connect the preamp to the component or circuit under test with, of course, shielded cable. Because the preamp input is DC-coupled, make sure the tested device has no more than  $\pm 300mV$  DC offset. (You can use a series 100nF blocking cap, but this increases preamp LF noise by about 0.4dB.)
2. Connect the preamp's output to a true-RMS AC voltmeter capable of reading down to at least 1mV. (With less sensitive meters you can use a post-amp, provided it's flat from 20Hz to 40kHz.)
3. Set the preamp's switches to 20Hz LFNBW, 20kHz HFNBW, and gain to 1000.
4. If the meter reads less than 200mV RMS, you can increase the gain to 10,000 without saturating the preamp's output.
5. Divide the measured voltage by the preamp gain; this is the component's unweighted 20Hz – 20kHz noise output.
6. Switch the "A" weighting on, and set the HFNBW to 100kHz (this makes the

response flat to 20kHz before the "A" filter, ensuring accurate "A" response). Divide the measured voltage by the preamp gain; this is the component's "A" weighted noise. The ratio of the component's maximum undistorted signal output to this noise in dB (20 times the log of this ratio) is the "A" weighted dynamic range. Using the component's nominal signal output (e.g., 1V RMS, 0.775V RMS, and so on) results in the "A" weighted SNR.

## VERY LOW NOISE MEASUREMENTS

With any component having at least 20dB gain, its amplified input noise will override this preamp's input noise, so that the preamp won't significantly contaminate the measurement. The preamp's 20Hz – 20kHz integrated noise is 147.7nV RMS on the proto unit, but it's subject to the LSK389B noise. The datasheet says  $0.9nV/\sqrt{Hz}$  typical, 2.5 maximum. I recommend using a DIP socket for Q1 so you can screen several JFETs for lowest noise.

In any case, noise levels below the preamp's own noise can be calculated by RMS subtraction:

1. Measure the preamp output noise while connected to the component under test.
2. Connect a shielded and shorted RCA plug to the preamp input, and again measure its output noise.
3. RMS subtract the two readings. For example, suppose the output with the component is 1.935mV, and with the input grounded it's 1.477mV (the proto unit with gain of 10,000).

Then square the 1.935, subtract 1.477 squared, and take the square root of the result: 1.250mV. Dividing this corrected output by the gain of 10,000 (used in this example) gives the component's noise, 125nV RMS, corrected for the preamp's own noise.

## POWER SUPPLY NOISE MEASUREMENTS

**Table 5** shows the noise of several DC power supplies, using the 100nF blocking cap cable. Noise from 20kHz – 100kHz (not shown) was much lower than audio band noise, except for the Marlin P. Jones unit (a 30V, 20A switching supply); switching at

**TABLE 3: PERFORMANCE DATA.**

Gain = 1000 or 10,000 (60 or 80dB)	
BW (-3dB) = 12.6Hz or 715Hz to 15.8kHz or 89.8kHz	
Noise BW = 20Hz or 1kHz to 20kHz or 100kHz	
Input noise voltage density =	1.045nV/ $\sqrt{Hz}$ , 20Hz-20kHz NBW average 0.972nV/ $\sqrt{Hz}$ , 1kHz-20kHz NBW average
Input Noise current density	$\leq 0.1pA/\sqrt{Hz}$
Total input noise voltage, 20Hz-20kHz =	147.7nV RMS (-136.6dBV)
same but "A" weighted =	111.5nV RMS (-139.0dBV)
Noise figure: 3.7dB (50 $\Omega$ ), 1.2dB (200 $\Omega$ ), 0.46dB (600 $\Omega$ ), 0.28dB (1k), 0.05dB (10k)	
Input impedance =	3.6M $\Omega$ //33pF
Output impedance =	200 $\Omega$
Maximum input voltage: $\pm 20mV$ DC $\pm 100mV$ DC	
Gain = 1000: 5mV RMS sine, 2.4mV RMS Gaussian noise	
Gain = 10,000: 0.5mV RMS sine, 0.24mV RMS Gaussian noise	
Maximum output voltage: 5.1V RMS sine, $\pm 72V$ peak, 2.4V RMS Gaussian noise	
THD (mostly 2nd harmonic): approximately 0.002%	
Battery supply: $\pm 9V$ at $\pm 21.2mA$	
External DC supply: $\pm 10V$ at $\pm 21.2mA$ , ground-isolated	

**TABLE 5: MEASUREMENT POWER SUPPLY NOISE.**

Power Supply	Vo io	RMS Output Noise		
		20Hz to 1kHz	1kHz to 20kHz	20Hz to 20kHz
LM317 C <sub>IN</sub> = 2mF, C <sub>ADJ</sub> = 0, C <sub>O</sub> = 10μF	+10V 32mA	65μV	206μV	216μV
LM337 C <sub>IN</sub> = 2mF, C <sub>ADJ</sub> = 0, C <sub>O</sub> = 10μF	-10V 32mA	74μV	202μV	215μV
LM317 C <sub>IN</sub> = 10mF, C <sub>ADJ</sub> = 10μF, C <sub>O</sub> = 10mF	+10V 32mA	40.0μV	19.6μV	44.6μV
LM337 C <sub>IN</sub> = 10mF, C <sub>ADJ</sub> = 10μF, C <sub>O</sub> = 10mF	-10V 32mA	18.5μV	25.2μV	31.3μV
Leader LPS - 152	+12V 200mA	38.4μV	7.6μV	39.2μV
Marlin P. Jones 1590PS	+30V 7.3A	295μV	78μV	305μV
Duracell 9V Alkaline Batteries MN1604 6LR61	+9V 9mA	<10nV	<10nV	<10nV

The AD797AN is available from Digi-Key (\$8.66) and Newark (\$8.84)

The LSK389B TO-71 is available from Linear Integrated Systems, (510) 490-9160

100kHz, the 20kHz – 100kHz noise is 670μV RMS.

The noise of the 9V alkaline battery was unmeasurable (with this preamp); it was no greater than the uncertainty of 10nV RMS. *ax*

## REFERENCE

1. Charles Hansen, “Noise Meter Amp,” *ax* Jan. ‘05.

**TABLE 4: PARTS LIST.**

Reference	Description	Size	Mfr.	P/N	Distributor	P/N
C14	cap, 14pF					
C22	cap, 33pF					
C13	cap, 56pF					
C7	cap, 68pF					
C20	cap, 200pF					
C6, 10	cap, 470pF					
C16	cap, 1.8nF, film	100V			DK	PS1182J
C11	cap, 2.0nF, film	100V			DK	PS1202J
C18	cap, 3.3nF, film	100V			DK	PS1332J
C21	cap, 4.7nF, film	100V			DK	PS1472J
C8, 9	cap, 10nF, film	100V			DK	PS1103J
C17	cap, 20nF	100V			DK	PS1203J
C12, 19	cap, 33nF, film	100V			DK	PS1333J
C15	cap, 100nF, film	100V			DK	PS1104J
C5	cap, 100μF	16V				
C1, 2, 4	cap, 1000μF	16V				
C3	cap, 2200μF	16V				
D1, 2	diode			1N4148		
D3, 4	diode			1N4001		
D5	Zener, 15V, 1W			1N4744A	DK	1N4744ADICT
J1, 4	phono jack, green				DK	CP-1417
J2, 3	phono jack, red				DK	CP-1413
LED1	LED, blue				DK	P466
R4	res, 1%MF, 10Ro	¼W				
R2	res, 15Ro	¼W				
R25, 26	res, 37R4	¼W				
R7	res, 182R	¼W				
R23	res, 200R	¼W				
R6	res, 511R	¼W				
R3	res, 866R	¼W				
R5	res, 1K18	¼W				
R24	res, 2k21	¼W				
R15	res, 3k01	¼W				
R9, 10	res, 4k99	¼W				
R13	res, 10ko	¼W				
R20, 22	res, 11k8	¼W				
R16, 17	res, 18k2	¼W				
R8	res, 51k1	¼W				
R14	res, 90k9	¼W				
R11, 18	res, 100k	¼W				
R12	Res, 1% MF, 200k	¼W				
R21	res, 237k	¼W				
R19	res, 1M00	¼W				
R1	Res, 10M, 5%	¼W				
S1-5	switch, DPDT, lock				DK	450-1487
TP1	trimpot, 1K				DK	3296Y-102
Q1	dual JFET	LS		LSK389B TO-71		
U1	op amp	AD		AD797 AN	DK	AD797AN
U2	dual op amp			TLO82CP	DK	296-1780-5
U3	op amp			TLO81CP	DK	296-7203-5
	box	Hammond		1590D	DK	HM154
	LED lens, blue				DK	L3006
	battery, 9V alkaline (2)					
	9V battery holder (2)				DK	BH9V-W
	8 pin DIP socket (4)				DK	A9408
	rubber bumper (4)	SPC		2567	Newark	92N4782

DK = Digi-Key, LS = Linear Systems, AD = Analog Devices